



Figure 3 You can further simplify the current sink's design by adding only two resistors, R_5 and R_6 , to the original in Figure 1. The output-current equation remains $I_{OUT} = (V_{REF}/R_1)$, as in Figure 2.