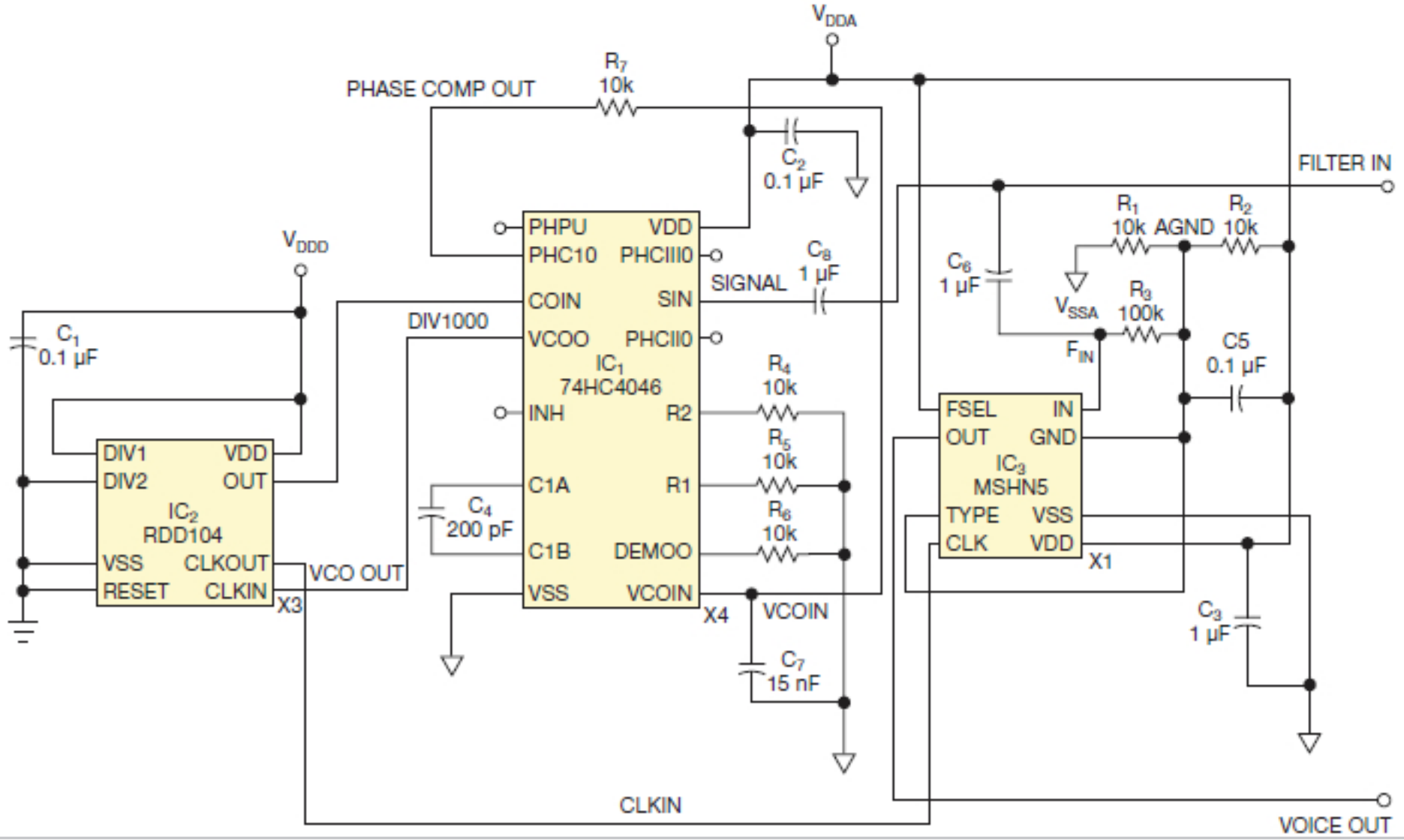

Figure 1 This audio notch-filter circuit uses a PLL to improve noise immunity.